

Roll No. Total Pages : 2

BCAR/M-14 939

LOGICAL ORGANIZATION OF COMPUTERS-II

Paper : BCA-122

(For Reappear Candidates)

Time : Three Hours] [Maximum Marks : 80

Note : Attempt *five* questions in all. Select *one* question from each unit. Q. No.1 is compulsory.

Compulsory Question

- 1. (a) Differentiate between Combinational and Sequential circuit. 3
- (b) Draw Excitation table of JKFF. 3
- (c) Define Access time and Seek time. 3
- (d) How JKFF is converted to D-FF ? 3
- (e) Define Interrupt and types of Interrupt. 3
- (f) How many FF are needed in Mod-10 counter ? 1

UNIT-I

- 2. Explain the problem associated with Clocked SRFF and discuss its solution. 16
- 3. Discuss Race-Around problem, and find solution for this. 16

UNIT-II

- 4. Explain Register to store 1010 in Parallel-in-Parallel-out mode. 16

939/1,800/KD/157

[P.T.O

- 5. (a) Make Excitation table of T-FF. 4
- (b) Make Mod-10 counter using T-FF. 12

UNIT-III

- 6. Define Memory. Explain Magnetic Disk on Secondary storage device. 16
- 7. (a) Discuss ROM and types of ROM.
- (b) Explain CD and DVD as storage media. 16

UNIT-IV

- 8. Explain Addressing modes and solve $x = (a - b) * (c + d)$ using 3, 2, 1, 0 addressings. 16
- 9. (a) Explain Cycle stealing.
- (b) Discuss Poll-driven data transfer. 16

http://www.kuonline.in

http://www.kuonline.in

http://www.kuonline.in

http://www.kuonline.in