

Roll No.

Total Pages : 3

BT-1/D-17**31022****BASICS OF ELECTRONIC ENGG.**

Paper : ECE-101(N)

Opt. (ii)

Time : Three Hours]

[Maximum Marks : 75

Note : Attempt *five* questions in all, selecting at least *one* question from each unit.

UNIT-I

1. (a) How zener diode is different from normal p-n diode ?
What are its applications? 7
- (b) Explain how zener diode can be used as a voltage regulator. 8

OR

2. (a) What is the use of Rectifiers? What are the various types of rectifiers ? 7
- (b) Explain the working of the full-wave bridge rectifier with necessary diagrams and waveforms. 8

UNIT-II

3. (a) Differentiate between Negative and Positive feedback. 7
- (b) What are the advantages of using negative feedback in amplifiers ? 8

31022/2,500/KD/1587


[P.T.O.]

OR

4. (a) Why Common Emitter (CE) is mostly used for making amplifiers ? 7
- (b) Explain the input and output VI characteristics of BJT CE configuration showing various regions of operation. 8

UNIT-III

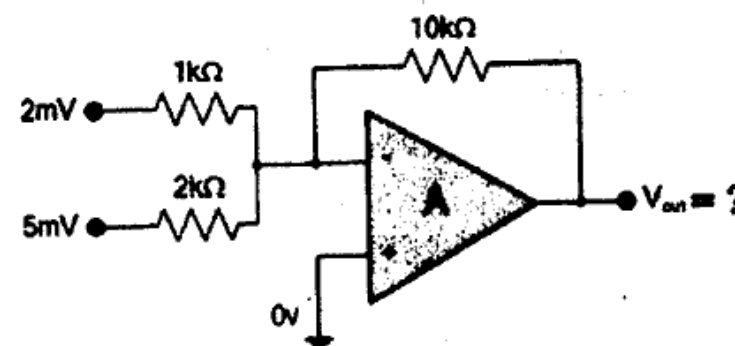5. (a) Prove that the output of the inverting Adder using Op-amp is $V_o = -R_f(V_1/R_1 + V_2/R_2)$. 8
- (b) Find the output of the adder circuit given in the following circuit : 7




OR

6. (a) Derive the output equations of the Inverting and non-inverting op-amp circuits. 8

31022/2,500/KD/1587

2

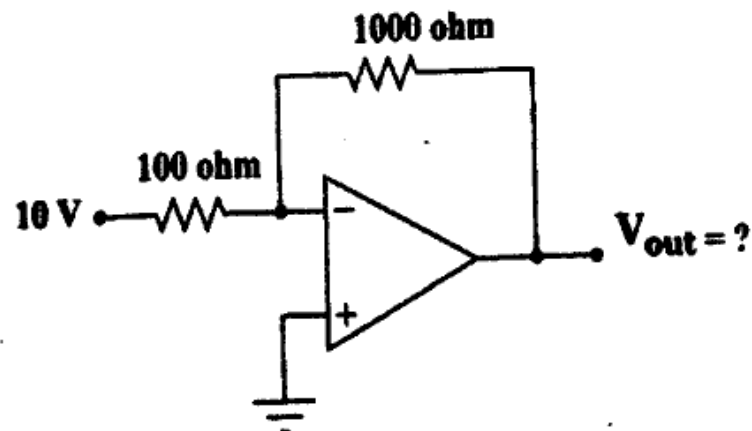- (b) Calculate the output of the following inverting op-amp circuit : 7



UNIT-IV

7. (a) Explain how UJT is different from BJT in operation and structure. 7
- (b) Describe the operation of UJT with its VI characteristics. What are its applications ? 8

OR

8. (a) What is TRIAC? How is it different from SCR? 7
- (b) Describe the operation and characteristics of TRIAC. What are its applications ? 8

<http://www.kuonline.in>

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से