

Roll No. ....

Total Pages : 04

**BT-2/M-17**                      **8206**  
**ELEMENTS OF ELECTRONICS**  
**ENGINEERING**  
**EL-101-e (Opt. i)**

Time : Three Hours]

[Maximum Marks : 75

**Note :** Q. No. 1 is compulsory. Attempt *Five* questions in all, with at least *one* question from each Unit. All questions carry equal marks.


1. Attempt all the questions :

- (i) Why the base terminal of BJT is made thinner than emitter and collector ?
- (ii) What is the relation between  $\alpha$  and  $\beta$  of BJT ?
- (iii) Why CE is mostly used for making amplifiers than CC and CB ?
- (iv) What are the *four* regions of operation of BJT in which it can operate ?
- (v) What are the advantages of using Negative feedback over Positive feedback ?
- (vi) What is Q-point ? What is its significance ?
- (vii) What are the various operations that can be performed by Op-Amp. ?

- (viii) What is significance of Slew Rate in Op-Amp. ?  
What is its value of Op-Amp 741 ?
- (ix) What is Common Mode Rejection Ratio ? For Noise reduction what is its ideal value ?
- (x) What is the value of threshold voltage for Si and Ge diodes.

**Unit I**

2. What is the use of rectifiers ? Explain the working of Full wave bridge rectifier and calculate its ripple factor.
3. What is the difference between clippers and clampers ?  
Find the output of the following clipper circuits ?

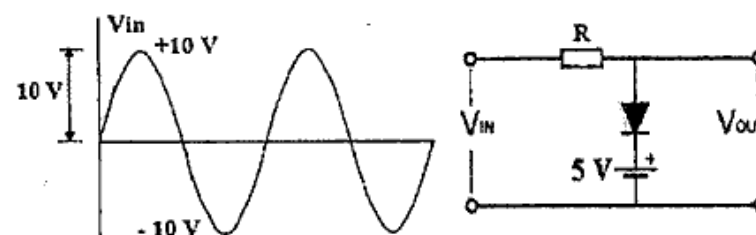


**Unit II**

4. Explain the input and output VI characteristics of common base BJT configuration showing four regions of operations ?


5. What is Barkhausen criterion of Oscillators? Explain the Wien Bridge Oscillator circuit and what is its frequency of oscillations ?

### Unit III

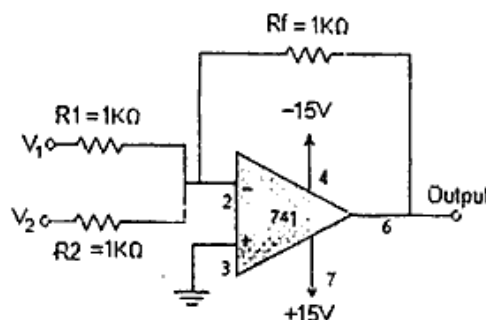6. How Op-Amp can be used as adder or summer ? Calculate the output of the following Op-Amp circuit ?



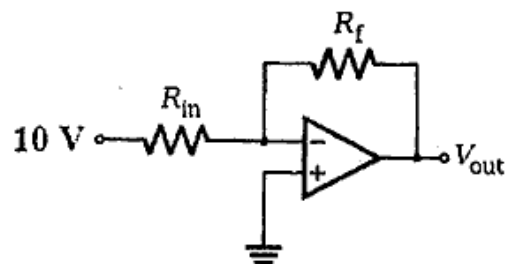7. How Op-Amp. can be used as inverter ? In the following circuit what should be the values of  $R_f$  and  $R_{in}$  into get output voltage of  $-100\text{ V}$  ?



### Unit IV

8. What is TRIAC ? Explain the working and operation of TRIAC ? What is its advantage over SCR ? 15
9. How JFET is different from MOSFET ? Explain the working and operation of JFET ? Explain the significance of Pinch-off voltage in the operation of n-channel JFET ?

15