

Roll No.

Total Pages : 2

BT-2/M-14

8222

**ELEMENTS OF ELECTRONICS
ENGINEERING**

Paper-EL-101-E

(2004-2007)

Option-I

Time Allowed : 3 Hours]

[Maximum Marks : 75

Note : Attempt five questions in all, selecting at least one question from each Unit. All questions carry equal marks.

UNIT-I

- Describe the working of Bridge Rectifier. 7
 - Explain Zener diode as a voltage regulator. 8
- Explain the operation of LED with its characteristics. 8
 - Determine V_0 for network of Fig. 1 for the input shown : 7

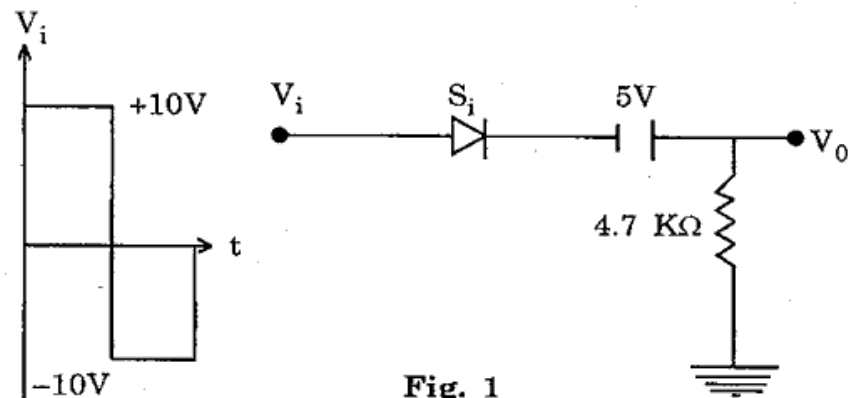


Fig. 1

8222/K/1552/550

P. T. O.

UNIT-II

- Explain the concept of d.c. and a.c. load line. How the operating point is selected? 15
- Find h_{re} in terms of the Common Base (CB) h-parameters. Also draw the CB hybrid model. 15

UNIT-III

- Explain the operational amplifier as differentiator. 8
 - Describe the working of differential amplifier and its transfer characteristics. 7
- Explain the operational amplifier as an integrator. 8
 - List the different characteristics of ideal Op-Amps. 7

UNIT-IV

- Explain the working of UJT. 8
 - Draw and explain the transfer characteristics of p-channel JFET. 7
- Write a short note on TRIAC. 8
 - Explain the working principle of p-channel enhancement type MOSFET. 7