http://www.kuonline.in

Roll	No.	***************************************	

Total Pages: 03

BT-3/D-14

8306

ANALOG COMMUNICATION ECE-203-E

Time: Three Hours] [Maximum Marks: 100

Note: Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

Unit I

- (a) What is Noise? Also mention its various sources.
 - (b) An antenna is connected to a receiver having an equivalent noise temperature of 100°K. The available gain of the receiver is 108 and noise bandwidth is 10MHz. If the available output noise power is 10 μW, determine the antenna temperature.
- (a) Analyze the addition of noise due to several sources.
 - (b) Determine noise bandwidth of a parallel RLC filter having a 3-dB bandwidth B.

(1-24) L-8306

P.T.O.

http://www.kuonline.in

Unit II

- (a) Draw the block diagram of a communication system and analyze the operation of its constituents.
 - (b) What is DSBSC? With the help an appropriate circuit diagram, explain a typical method of achieving DSBSC.
- 4. (a) Draw the circuit diagram of a diode detector and explain its operation giving the respective waveforms. Also explain how you will set the value of RC time constant in this detector.
 - (b) What is Vestigial side band transmission? How will you achieve this transmission?

Unit III

- (a) Define Frequency Modulation. Also illustrate the relationship between phase and frequency modulation.
 - (b) Draw the block diagram of an Indirect Method of frequency modulation and analyze its operation.

L-8306

2

http://www.kuonline.in

- 6. (a) With appropriate diagram, explain the operation of pre-emphasis circuit.
 - (b) An FM carrier is sinusoidal modulated.

 Determine those values of modulation index for which all the power will lie in the sidebands.

Unit IV

- (a) Give the block diagram of an AM transmitter and explain the function of its constituents.
 - (b) Discuss the following:
 - (i) Frequency scintillation
 - (ii) Frequency drift.
- 8. (a) Draw the block diagram of simple FM transmitter using reactance modulator and explain its working.
 - (b) Write a detailed note on the tracking and alignment of receivers.