

Roll No. ....

Total Pages : 3

BT-3/DX

8310

SEMICONDUCTOR DEVICES AND CIRCUITS

Paper : ECE-201(E)

Time : Three Hours]

[Maximum Marks : 100

**Note :** Attempt *five* questions in all, selecting at least *one* question from each unit.

**UNIT-I**

1. (a) Explain the following :
  - (i) Reverse saturation current.
  - (ii) Cut-in voltage.
  - (iii) Forward biasing.
  - (iv) Reverse biasing.  $2\frac{1}{2} \times 4 = 10$
- (b) What are various Filter circuits ? Explain, what are their applications. 10
2. (a) Explain the following :
  - (i) Ripple factor.
  - (ii) Average voltage.
  - (iii) Form factor.
  - (iv) Voltage regulation.  $2\frac{1}{2} \times 4 = 10$
- (b) Draw and explain the circuit of a Series voltage regulator and compare it with the features of Shunt voltage regulator. 10

**UNIT-II**

3. (a) Draw the hybrid model of a transistor. Obtain  $h$ -parameters for a CE stage amplifier. 10
- (b) What is the need of biasing the transistor ? Explain self-bias circuit. 10
4. (a) Explain transistor RC coupled amplifier with special reference to frequency response, advantages, disadvantages and applications. 10
- (b) What is the dB gain of an amplifier for an increase of power level from 12 W to 24 W ? 10

**UNIT-III**

5. (a) The overall gain of a multistage amplifier is 140. When negative voltage feedback is applied, the gain is reduced to 17.5. Find the fraction of the output that is fed back to the input. 10
- (b) What is Barkhausen's criterion ? Where is it applied ? 10
6. (a) What are the advantages and disadvantages of feedback in amplifiers ? Explain. 10
- (b) What are Oscillators ? How do they produce oscillations ? Explain the circuit of Wein Bridge oscillator. What is its frequency ? 10

**UNIT-IV**

7. (a) Explain a depletion mode MOSFET with its construction and characteristics. 10
- (b) When  $V_{GS}$  of a JFET changes from  $-3.1$  V to  $-3$  V, the drain current changes from  $1$  mA to  $1.3$  mA. Calculate the value of transconductance. 10
8. Write short notes on the following :
- (a) Small signal model of JFET. 10
- (b) Biasing of MOSFETs. 10
-