

Roll No.

Total Pages : 3

GSE/M-20

1457

COMPUTER SCIENCE
(Logical Organisation of Computer)
Paper-II

Time : Three Hours]

[Maximum Marks : 25

Note : Attempt *five* questions in all. Question No. 1 is compulsory.

Select *one* question from each section.

Compulsory Question

1. Answer in short :

- (i) Abbreviate ASCII, BCD. (1)
- (ii) Define Duality principle. (1)
- (iii) Discuss Half Adder. (1)
- (iv) Make table for self-complementing code. (1)
- (v) Explain Race-around problem. (1)

SECTION-I

2. Convert the following :

- (i) $(7.3)_{10} = (\dots)_2$ (1)
- (ii) $(1101110110)_2 = (\dots)_8$ (1)

(iii) $(10.625)_{10} = (\dots)_{16}$ (1)

(iv) $(10.3)_{10} = (\dots)_8$ (2)

3. Write notes on the following :

(i) Error detection and correction. (2½)

(ii) Floating point representation. (2½)

SECTION-II

4. (i) Define Boolean Algebra and write its postulates. (2)

(ii) Solve using Boolean Algebra :

$$XY + \overline{X}Z + YZ = XY + \overline{X}Z. \quad (1\frac{1}{2})$$

$$ABC + A\overline{B}C + AB\overline{C} + A\overline{B}\overline{C} = A. \quad (1\frac{1}{2})$$

5. (i) Solve using k -map :

$$Z = \Sigma(0, 2, 3, 7, 9) + \sum_{\phi}(1, 4, 5, 11) \quad (2\frac{1}{2})$$

(ii) Draw and label 4-variable k -map. (2½)

SECTION-III

6. (i) Prove that NAND, NOR are universal gates. (2½)

(ii) Draw the circuits for following :

$$X = (\overline{A}B + A\overline{B})CD + \overline{XYZ}. \quad (2\frac{1}{2})$$

7. (i) Design 4 : 1 multiplexer. (2½)
(ii) Design 10 to 4 line encoder. (2½)

SECTION-IV

8. Draw the logic diagram of *RS* flip flop and explain its working and find its equation. (5)
9. Explain the working of Serial Input Serial Output (SISO) and Serial Input parallel Output Register. (5)
-