

Roll No.

Total Pages : 4

GSE/M-20

1493

ELECTRONICS-I

(Electronic Devices and Circuits-II)

Paper-I

Time : Three Hours]

[Maximum Marks : 40

Note : Attempt *five* questions in all, selecting *one* question from each unit. Question No. 1 is compulsory.

Compulsory Question

1. (a) How a FET can be used as a voltage-variable resistance ?
(b) What is the condition for thermal stability ?
(c) What is the need of coupling in a multistage amplifier ?
(d) What is thermal runaway ? How is it related to the biasing of a transistor ? (2×4=8)

UNIT-I

2. (a) Show that the stability factor for the collector to base

$$\text{bias is } s = \frac{(1 + \beta)}{\left[1 + \frac{\beta R_c}{R_B + R_c}\right]} \text{ and } s' = \frac{-\beta.s}{(1 + \beta)(R_B + R_c)}.$$

5

- (b) Explain why biasing is necessary in an amplifier ? 3

3. (a) For the collector to base bias circuit, the BJT used is specified to have β values in the range of 20 to 200. If feedback resistance is $100\text{ k}\Omega$ and emitter resistance is $1\text{ k}\Omega$, for the two extreme values of β (20 & 200), find V_E , I_E and V_B . 4
- (b) The operating point is required to be selected in the middle of load line in an amplifier circuit. Why ? What are the reasons due to which Q-point gets shifted ? Explain. 4

UNIT-II

4. (a) A 50-NPN transistor is used in self-bias CE amplifier, having $\beta = 50$ at room temperature. The circuit has $R_1 = 90\text{ k}\Omega$ and $R_2 = 10\text{ k}\Omega$ and $R_E = 1.5\text{ k}\Omega$. The values of other components are adjusted to have the collector current $I_C = 2\text{ mA}$. Calculate the values of s , s' , s'' . 5
- (b) Why thermal runaway cannot take place, if $V_{CE} < \frac{V_{CC}}{2}$. 3
5. (a) Draw a self-bias circuit. Explain qualitatively why such a circuit is an improvement on the fixed bias circuit, as for as stability is concerned. How is the load line drawn for a self-bias circuit ? 4
- (b) The mid frequency gain of a RC coupled amplifier is 100. The values of higher and lower cut off frequencies are 100 kHz and 100 Hz , respectively. Find the frequency at which the gain reduces to 80. 4

UNIT-III

6. (a) The h -parameters of the transistors used in two stage RC coupled amplifier are $h_{fe} = 400$, $h_{ie} = 8 \text{ k}\Omega$. If the shunt capacitance at high frequency is 500 pf, coupling capacitance is $0.5 \text{ }\mu\text{F}$ and $R_L = 15 \text{ k}\Omega$, calculate the lower and higher cut off frequencies of the amplifier. The source may assume to be negligibly small. 5
- (b) Outline the general method for obtaining the high frequency response of two interacting amplifier stages. 3
7. (a) Sketch the response of an amplifier to a low frequency square wave. What is tilt and how is it related to the low 3-dB frequency f_L ? 4
- (b) For an RC coupled amplifier, the mid frequency gain is 200. If the gain falls by 6 dB at the lower cut off frequency, calculate the gain at the cut-off frequency in dB. 4

UNIT-IV

8. (a) If two identical FET, are connected in parallel then prove that the effective transconductance is doubled and drain resistance is halved. The amplification factor remains unchanged. 4
- (b) A common source amplifier uses FET having $\gamma_d = 10 \text{ k}\Omega$ and $\mu = 16$. Calculate the voltage and output resistance of the amplifier for load resistance equal to (i) $100 \text{ k}\Omega$ (ii) $200 \text{ k}\Omega$ (iii) $1 \text{ M}\Omega$. 4

9. (a) A common source FET amplifier uses load resistance $R_L = 100 \text{ k}\Omega$ and an unbypassed resistance R_s connected between source and ground. The γ_d of FET is $200 \text{ k}\Omega$ and $g_m = 0.1 \text{ m}\Omega^{-1}$. Compute the voltage gain and output resistance of the amplifier for R_s equal to : (i) $5 \text{ k}\Omega$ (ii) $50 \text{ k}\Omega$ (iii) $20 \text{ k}\Omega$. 4
- (b) Draw the small signal model of a FET and show that the FET behaves as a voltage controlled current source (VCCS). 4
-