

Roll No. ....

Total Pages : 3

**BAM/A-20**  
**ELECTRONICS**  
**Paper-II (Theory)**

**564**

Time : Three Hours]

[Maximum Marks : 45

**Note :** Attempt *five* questions in all, selecting *one* question from each unit. All questions carry equal marks.

**UNIT-I**

1. (a) What is Combinational circuit ? Explain the full adder circuit with the help of truth table. 5  
(b) Implement the full adder circuit using
  - (i) Half adders.
  - (ii) NAND gates. 4
2. (a) What is Multiplexer circuit ? Explain a 8 : 1 multiplexer with the help of its truth table and its circuit using NAND gates. 6  
(b) Implement the following boolean function using a 8 : 1 multiplexer :
$$f(A, B, C) = \Sigma(0, 2, 5, 7).$$
 3

**UNIT-II**

3. (a) What is Flip-flop ? Explain the working of JK flip-flop with the help of its circuit diagram and truth table. 6

- (b) What are the salient features of 1-bit memory cell ? 3
4. (a) Design a 4-bit Asynchronous counter using T flip-flops.  
Give its truth table and output waveforms. 6
- (b) Make the state diagram of above counter [Part-(a)]  
showing all the necessary signals. 3

### **UNIT-III**

5. What do you understand by Shift register ? How many different types of shift registers are there ? Explain a 4-bit SISO shift register with the help of its circuit diagram and output waveforms. 9
6. What is Ring Counter ? Explain the working of 4-bit Ring counter with the help of its output waveforms. 9

### **UNIT-IV**

7. Why a D/A converter is required ? Explain the working of 4-bit weighted resistor D/A converter with the help of its neat and clean diagram. What are its limitations ? 9
8. Why a A/D converter is required ? Explain the working of 4-bit simultaneous A/D converter with the help of its circuit diagram. What are its merits and demerits ? 9

### **UNIT-V**

9. (a) Define Frequency modulation, and derive an expression for the frequency modulated carrier wave and also define the modulation index. 6

- (b) What are the advantages of FM over AM ? 3
- 10.** (a) What do you understand by Differential PCM (DPCM) ?  
Explain with the help of circuit diagram that how DPCM  
is different from PCM. 5
- (b) What do you understand by a Sample and Hold circuit  
(S/H) ? Explain with the help of its circuit diagram,  
input and output waveforms. 4
-