

Roll No. ....

Total Pages : 2

**BT-1/D-18**

**31012**

**ELECTRICAL TECHNOLOGY**

Paper : EE-101(E)

Opt. (II)

Time : Three Hours]

[Maximum Marks : 100

**Note :** Attempt five questions in all, selecting at least one question from each of the four Sections A, B, C and D.

**SECTION-A**

1. (a) Explain in detail the theory of AC response of series RC circuit with neat diagrams. 10
- (b) Draw neatly the waveforms on simultaneous time scale :  
 $V_1 = V_m \sin \omega t$ ,  $V_2 = V_m (\sin \omega t - 120^\circ)$ ,  
 $V_3 = V_m (\sin \omega t - 240^\circ)$  in volts. 10
2. Write short notes on the following :
  - (a) Ohm's law. 5
  - (b) Rectangular form of representing a Phasor quantity. 5
  - (c) Polar form of representing a Phasor quantity. 5
  - (d) RMS value of a waveform. 5


**SECTION-B**

3. (a) Explain Maximum power transfer theorem and establish its condition. 15
- (b) Explain cut-off frequencies and bandwidth in case of series RLC circuit. 5

31012/3,500/KD/2191

[P.T.O.  
29/12

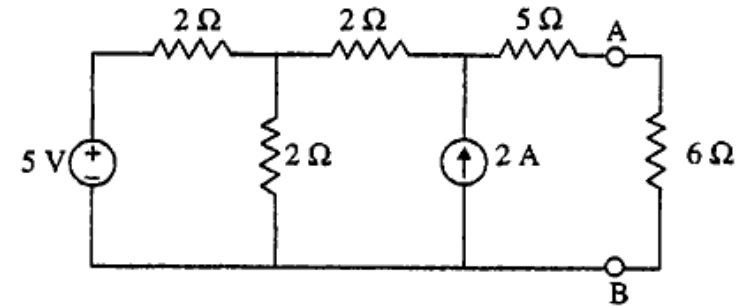4. Find Norton's equivalent of the given circuit w.r.t. 6 Ω resistor and find the current in 6 Ω resistor. 20



**SECTION-C**

5. Establish the relations between :
  - (a) Line voltage and phase voltage in a star connected 3-phase system. 10
  - (b) Line current and phase current in a delta connected 3-phase system. 10
6. (a) Explain O/C and S/C tests in a single phase transformer with the help of neat sketches. 15
- (b) Explain transformer at no load with phasor diagram. 5

**SECTION-D**

7. Explain how is a 3-phase pulsating magnetic flux equivalent to a bipolar revolving flux with the help of neat sketches. How this concept is used to explain working of 3-phase induction motor? 20
8. Explain principle, general construction and working of DC motor with suitable sketches. 20

31012/3,500/KD/2191

2