

Roll No.

Total Pages : 03

BT-2/M-19 32006
ELEMENTS OF ELECTRONICS
ENGINEERING
EL-101E (Opt. II)

Time : Three Hours]

[Maximum Marks : 75

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit. Q. No. 1 is compulsory. All questions carry equal marks.

1. (a) What is the difference between clippers and clampers ?
- (b) Draw the equivalent model of Op-Amp 741.
- (c) Explain the difference between Active and Passive electronic components.
- (d) What is the use of filters in rectifiers ?
- (e) What is a Rectifier ? What are its types ? $5 \times 3 = 15$

Unit I

2. Explain the operation of Full-Wave bridge rectifier with necessary diagram. Why Full-wave bridge rectifier is preferred over centre-tapped rectifier for making regulated power supply ? 15

(3-43/9) L-32006

P.T.O.

3. What is the use of clippers in electronics circuits ? What are the types of clippers ? Differentiate between positive and negative clippers with examples. 15

Unit II

4. Explain the input and output characteristics of Common Base (CB) BJT amplifier configuration with necessary V-I graphs indicating four regions of operation. 15
5. What is the need of biasing in BJT ? Explain the various biasing configuration with necessary diagrams. 15

Unit III

6. Explain the inverting, non-inverting and different modes of Op-Amp with necessary diagrams. Explain, how Op-Amp can be used to produce an output of 10 V for an input of 5 V. Which configuration will be used for this ? <http://www.kuonline.in> 15
7. Derive the expression of differentiator using Op-Amp ? Explain, how it will produce a square waveform as output for a Triangular wave input ? 15

L-32006

2

Unit IV

8. What is a SCR ? Explain the operation and characteristics of SCR with necessary diagrams. Describe the applications of SCR. **15**
9. What is MOSFET ? How is it different from FET ? Explain its structure, working, characteristics and applications with necessary graphs and disadvantages. **15**

<http://www.kuonline.in>

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से