

Roll No.

Total No. of Pages : 2

BT-3/D11**7606****Semiconductor Devices and Circuits****Paper : ECE-201 E**

Time : Three Hours]

{Maximum Marks : 100

Note :- Attempt any FIVE questions.

1. (a) How does a PN Junction work as a rectifier ? Compare rectifier circuits. 10
(b) Explain photoelectric devices and their principle of working. 10
2. (a) Draw a series voltage regulator. How does it work ? 10
(b) Draw block diagram of SMPS. Explain its working. 10
3. Explain the following :-
 - (a) Miller's theorem
 - (b) Early effect in transistors
 - (c) Hybrid model of a transistor
 - (d) Thermal runaway in transistors. $5 \times 4 = 20$
4. Explain the following :-
 - (a) Bias Compensation
 - (b) Thermistor
 - (c) High frequency limitation of BJT
 - (d) Emitter follower. $5 \times 4 = 20$
5. (a) What is the need of feedback ? What is its impact on input resistance, gain, Bandwidth and output impedance ? 10
(b) Draw various feedback topologies. What are their applications ? Compare their features. 10

6. (a) What are various amplifiers ? Compare their features and obtain their efficiencies. 10
(b) Draw circuit of a crystal oscillator. How does it work ? How is it better than weinbridge oscillator ? 10
7. (a) Draw the construction of a V-MOSFET. How does it work ? What are its applications ? 10
(b) Write short notes on enhancement type MOSFET. 10
8. Explain the following terms and write short notes on :-
 - (a) Biasing of MOSFETS 10
 - (b) JFET. 10