

Roll No.

Total Pages : 03

BT-7/D-19 37134
POWER ELECTRONICS
ECE-405N (Option I)

Time : Three Hours]

[Maximum Marks : 75

Note : Attempt exactly *Five* questions by selecting at least *one* question from each of the four Sections A, B, C and D.

Section A

1. Explain the static and switching characteristics of IGBT & MOSFET and critically compare the two. 15
2. (a) What do you mean by the following terms and write down the purpose of each ?
 - (i) Converter
 - (ii) Inverter
 - (iii) Chopper
 - (iv) Cycloconverter
 - (v) AC Controller 2×5=10
- (b) Define the following :
 - (i) firing angle
 - (ii) commutation 5

(4-02/13) L-37134

P.T.O.

Section B

3. (a) Draw the cross sectional structure of general purpose Thyristor. Explain the latching and holding currents of SCR. 10
- (b) Comment on the statement : 'When subjected to standby increasing over voltages, the thyristor needs over current protection but not overvoltage protection.' 5
4. (a) Discuss briefly the voltage commutation and current commutation techniques used for the commutation of thyristors. 10
- (b) Compare GTO and general purpose thyristor. Give typical applications of GTO. 5

Section C

5. (a) How are choppers classified ? Briefly explain the operation of a type-C chopper. 10
- (b) Explain voltage control in single phase inverters. 5
6. (a) Explain time ratio control (TRC) and current limit control strategies employed for d.c. choppers. Also, enumerate applications and limitations of individual strategies. 10
- (b) Explain, with a diagram, how a step-up chopper works. 5

L-37134

2

Section D

7. (a) Explain the principle of load commuted Cycloconverter and discuss its advantages and disadvantages over line commuted converters. **10**
- (b) Briefly explain the operation of a single-phase Cycloconverter which accepts 230 V/50 Hz a. c. and provides output voltage at 16.6 Hz. **5**
8. (a) Explain the operation of a single-phase to single phase step-down Cycloconverter with suitable sketches. Assume resistive load. **12**
- (b) What are the applications of Cycloconverter ? **3**